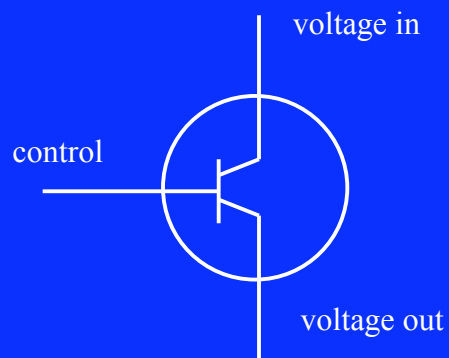


Transistors and Logic Circuits


Transistor



control high allows
current to flow --
switch is closed (on)

control low stops
current flow
switch is open (off)


NOT Gate One transistor

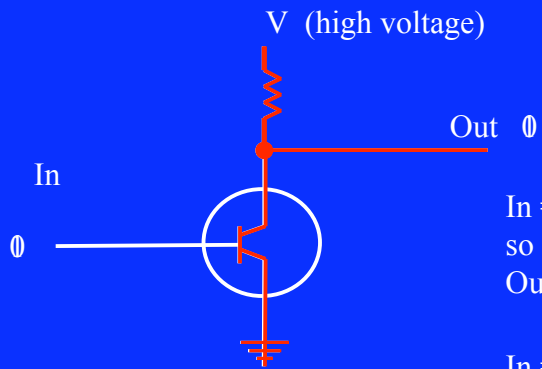

In = high, switch is closed
so current flows to ground
Out is low.

In = low, switch is open
so current flows to Out
Out is high.

NOR Gate Two transistors

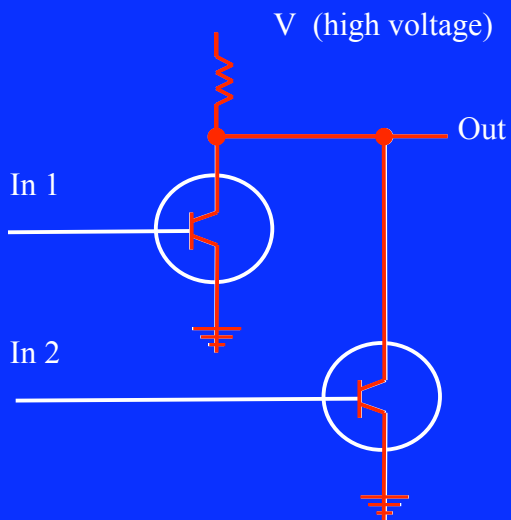


In 1 = 1, Out = 0

In 2 = 1, Out = 0


In 1 = 0

In 2 = 0, Out = 1

NAND Gate Two transistors

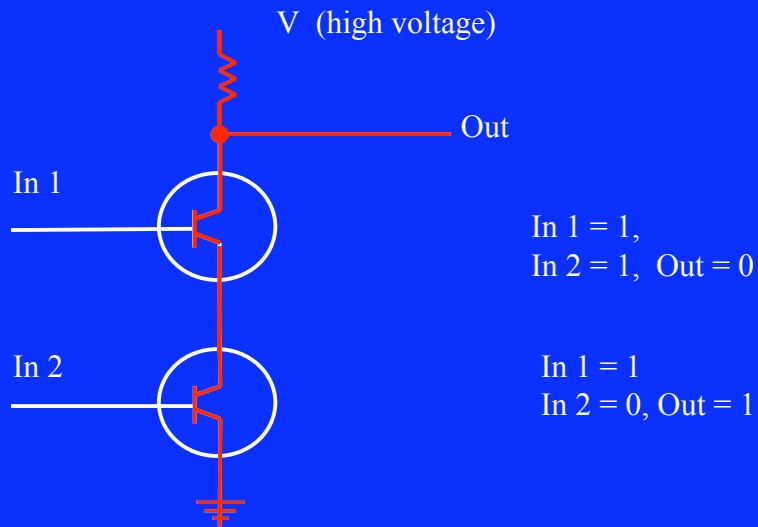


AND Gate Three transistors

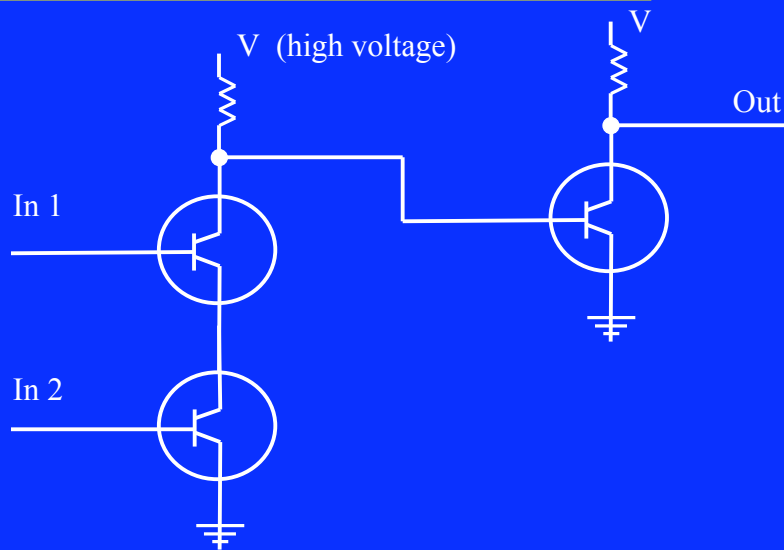


Logic Gates




Logic Circuit -- 4 input Multiplexor

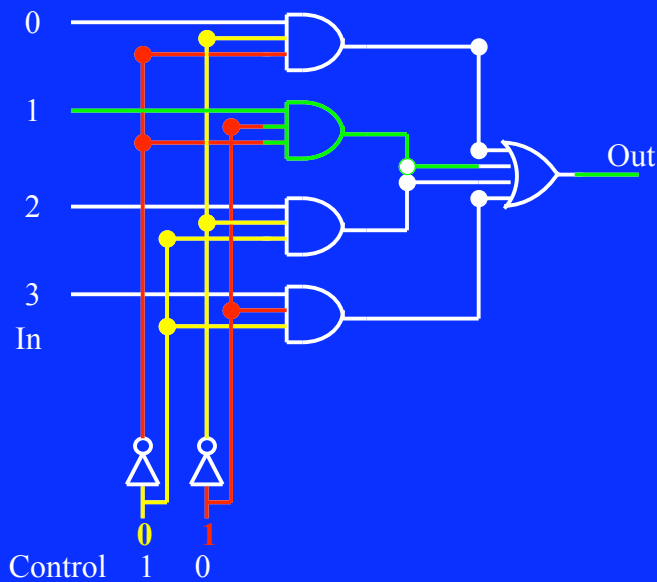

Logic Circuit Puzzle 1

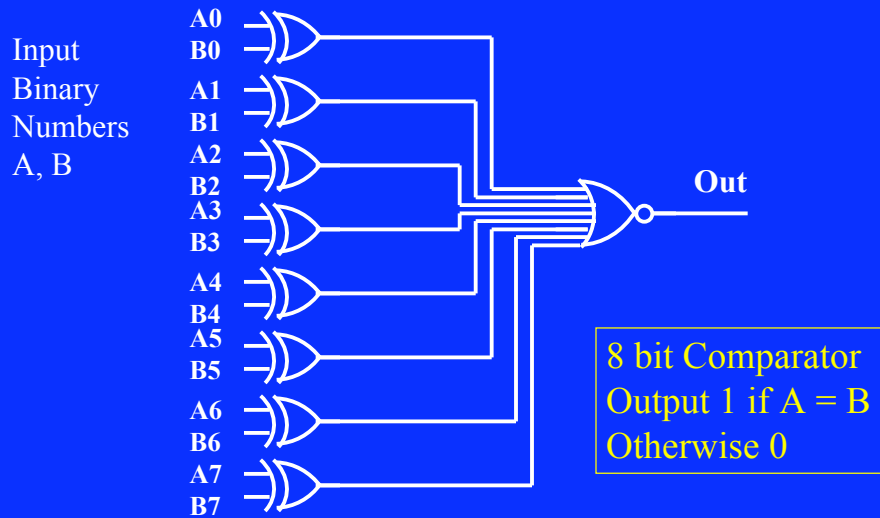

Logic Circuit Puzzle 2

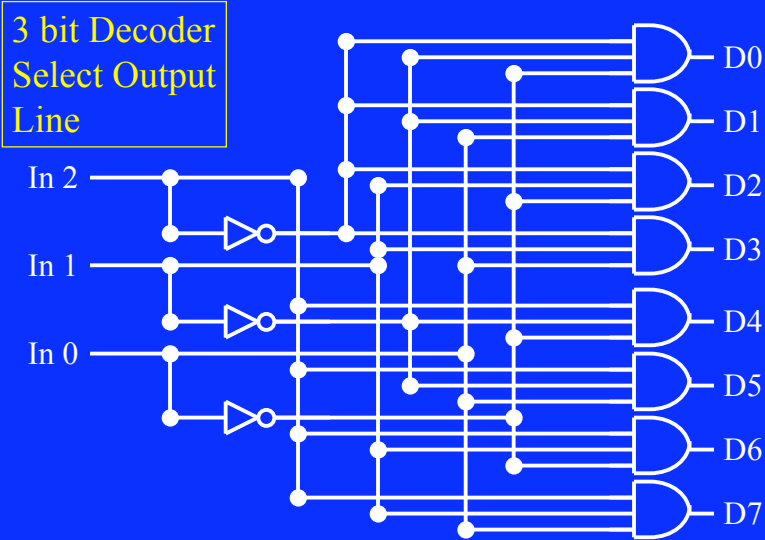


Programmable Logic Array

- Any Logic Truth Table can be implemented
- Uses block of AND gates followed by block of OR gates
- Programmable
 - once
 - many times
- Used for implementing different circuits


Truth Table to Normal Form

A	B	C	expression	A and B and C
1	1	1	1	A and B and ~C
1	1	0	1	A and ~B and C
1	0	1	1	~A and B and C
1	0	0	0	
0	1	1	1	
0	1	0	0	
0	0	1	0	
0	0	0	0	
<hr/>				
0	$(A \text{ and } B \text{ and } C) \text{ or } (A \text{ and } B \text{ and } \sim C)$ $\text{or } (A \text{ and } \sim B \text{ and } C) \text{ or } (\sim A \text{ and } B \text{ and } C)$			

PLA

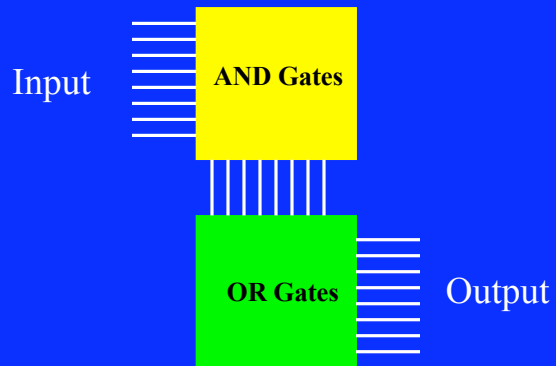

PLA

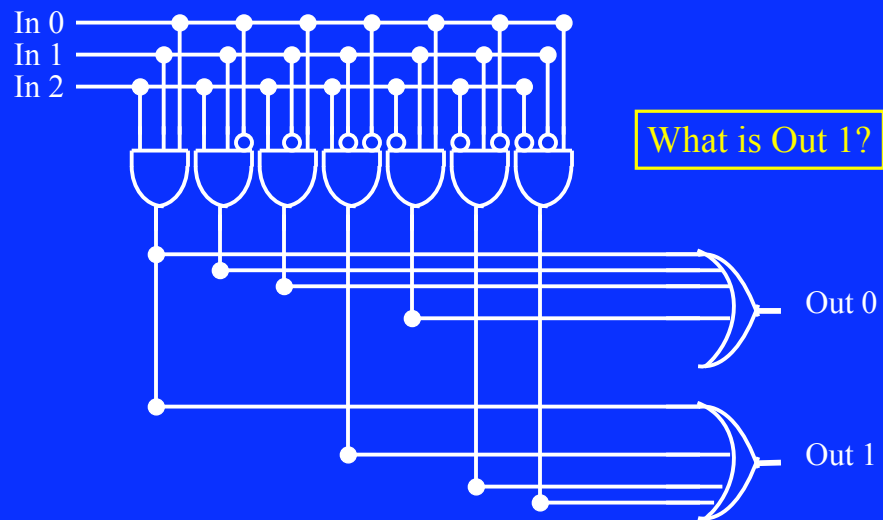

Normal Form to Truth Table

A	B	C	expression
1	1	1	1 A and B and C
1	1	0	0 Odd Parity
1	0	1	0
1	0	0	1 A and ~B and ~C
0	1	1	0
0	1	0	1 ~A and B and ~C
0	0	1	1 ~A and ~B and C
0	0	0	0

(A and B and C) or (A and ~B and ~C)
or (~A and B and ~C) or (~A and ~B and C)


PLA, Alternate Representation

AND Block uses DeMorgan Equivalence


$A \text{ and } B = \text{not}(\text{not } A \text{ or not } B)$




OR Block uses direct or

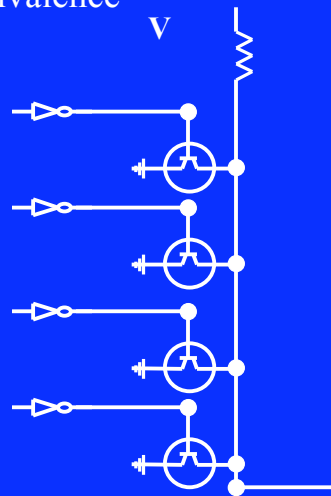

PLA, Alternate Representation

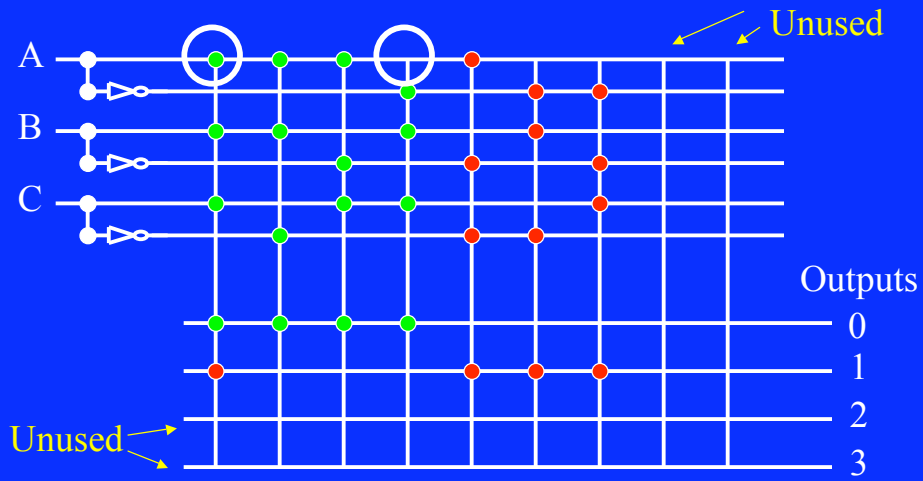

PLA, Alternate Representation

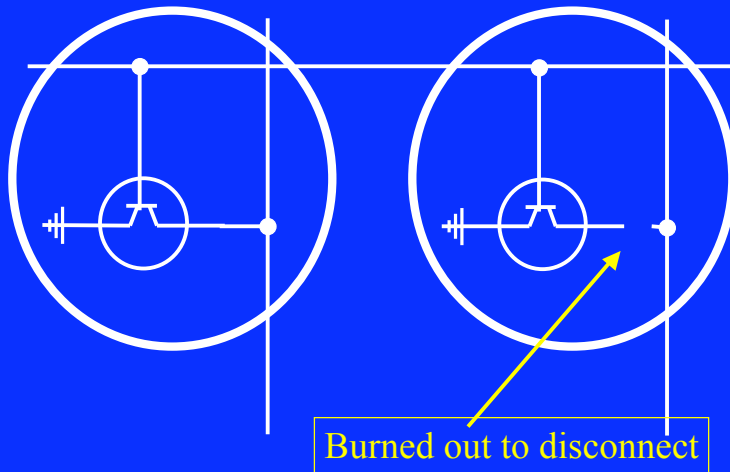


PLA "Don't Cares"

A	B	C	exp		A	B	C	exp
1	1	1	1	→	1	1	X	1
1	1	0	1	→				
1	0	1	1		1	0	1	1
1	0	0	0		1	0	0	0
0	1	1	1		0	1	1	1
0	1	0	0		0	1	0	0
0	0	1	0		0	0	1	0
0	0	0	0		0	0	0	0

X = Don't Care

PLA "Don't Cares"

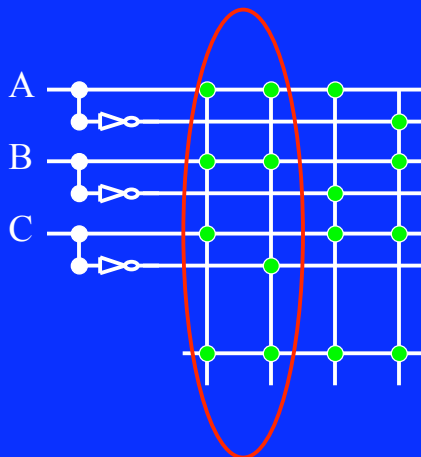

Reduce number of PLA lines used for expression

