

Single Cycle Implementation Cycle Time

- ❑ Unfortunately, though simple, the single cycle approach is not used because it is very slow
- ❑ Clock cycle must have the same length for every instruction
- ❑ What is the longest (slowest) path (slowest instruction)?

Instruction Critical Paths


- ❑ Calculate cycle time assuming negligible delays (for muxes, control unit, sign extend, PC access, shift left 2, wires, setup and hold times) except:

- Instruction and Data Memory (200 ps)
- ALU and adders (100 ps)
- Register File access (reads or writes) (100 ps)

| Instr. | I Mem | Reg Rd | ALU Op | D Mem | Reg Wr | Total |
|--------|-------|--------|--------|-------|--------|-------|
| R-type | 200 | 100 | 100 | | 100 | 500 |
| load | 200 | 100 | 100 | 200 | 100 | 700 |
| store | 200 | 100 | 100 | 200 | | 600 |
| beq | 200 | 100 | 100 | | | 400 |
| jump | 200 | | | | | 200 |

Single Cycle Disadvantages & Advantages

 - ❑ Uses the clock cycle inefficiently – the clock cycle must be timed to accommodate the **slowest** instr
 - especially problematic for more complex instructions like floating point multiply




- ❑ May be wasteful of area since some functional units (e.g., adders) must be duplicated since they can not be shared during a clock cycle but
- ❑ It is simple and easy to understand

Multicycle Implementation Overview


- ❑ Each instruction **step** takes 1 clock cycle
 - Therefore, an instruction takes **more** than 1 clock cycle to complete
- ❑ Not every instruction takes the **same** number of clock cycles to complete
- ❑ Multicycle implementations allow
 - faster clock rates
 - different instructions to take a different number of clock cycles
 - functional units to be used more than once per instruction as long as they are used on different clock cycles, as a result
 - only need one memory
 - only need one ALU/adder

The Multicycle Datapath – A High Level View

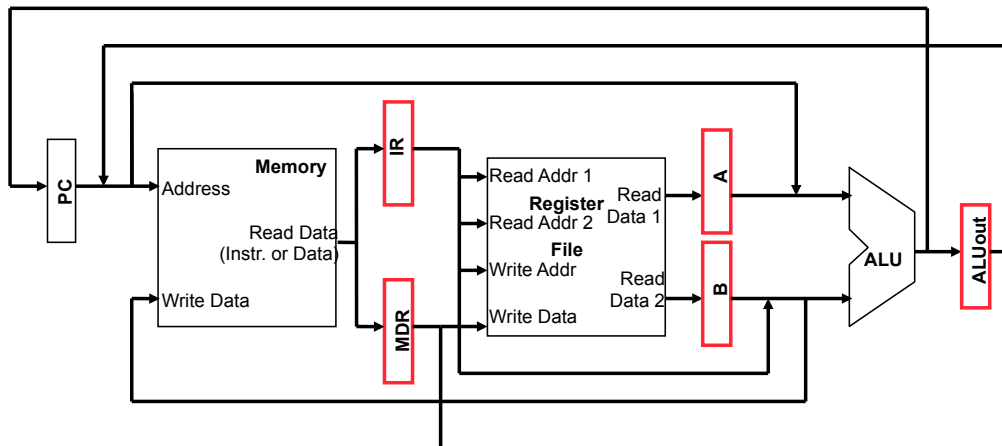- ❑ Registers have to be added after every major functional unit to hold the output value until it is used in a subsequent clock cycle




Clocking the Multicycle Datapath

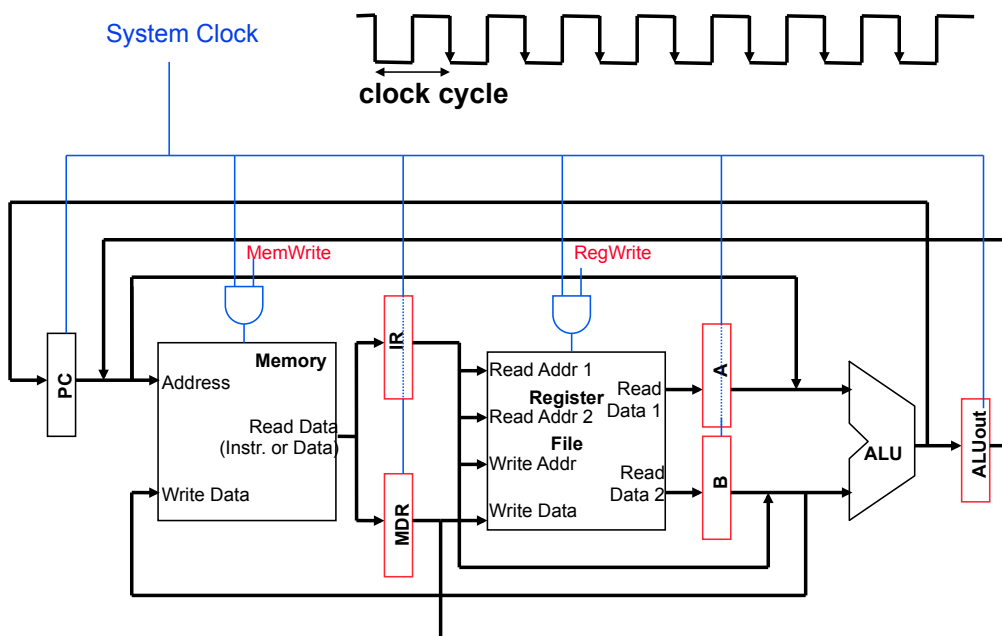

Our Multicycle Approach

- ❑ Break up the instructions into steps where each step takes a clock cycle while trying to
 - balance the amount of work to be done in each step
 - use only one major functional unit per clock cycle
- ❑ At the end of a clock cycle
 - Store values needed in a later clock cycle by the **current** instruction in a state element (internal register not visible to the programmer)
 - IR – Instruction Register
 - MDR – Memory Data Register
 - A and B – Register File read data registers
 - ALUout – ALU output register
 - All (except **IR**) hold data only between a pair of adjacent clock cycles (so they don't need a write control signal)
 - Data used by subsequent instructions are stored in programmer visible state elements (i.e., Register File, PC, or Memory)

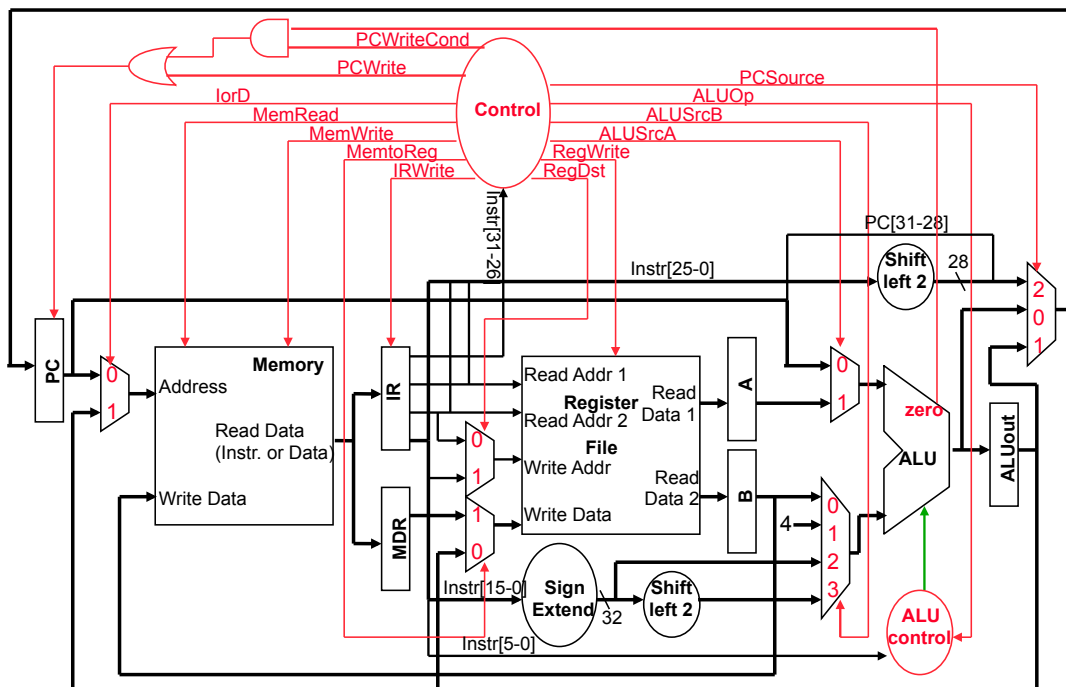The Complete Multicycle Data with Control



Review: Our ALU Control

□ Controlling the ALU uses of multiple decoding levels

- main control unit generates the **ALUOp bits**
- ALU control unit generates **ALUcontrol bits**

| Instr op | funct | ALUOp | action | ALUcontrol |
|----------|--------|-------|----------|------------|
| lw | xxxxxx | 00 | add | 0110 |
| sw | xxxxxx | 00 | add | 0110 |
| beq | xxxxxx | 01 | subtract | 1110 |
| add | 100000 | 10 | add | 0110 |
| subt | 100010 | 10 | subtract | 1110 |
| and | 100100 | 10 | and | 0000 |
| or | 100101 | 10 | or | 0001 |
| xor | 100110 | 10 | xor | 0010 |
| nor | 100111 | 10 | nor | 0011 |
| slt | 101010 | 10 | slt | 1111 |

Our Multicycle Approach, con't

- Reading from or writing to any of the internal registers, Register File, or the PC occurs (quickly) at the beginning (for read) or the end of a clock cycle (for write)
- Reading from the Register File takes ~50% of a clock cycle since it has additional control and access overhead (but reading can be done in parallel with decode)
- Had to add multiplexors in front of several of the functional unit input ports (e.g., Memory, ALU) because they are now shared by different clock cycles and/or do multiple jobs
- All operations occurring in one clock cycle occur in parallel
 - This limits us to one ALU operation, one Memory access, and one Register File access per clock cycle

Five Instruction Steps

1. Instruction Fetch
2. Instruction Decode and Register Fetch
3. R-type Instruction Execution, Memory Read/Write Address Computation, Branch Completion, or Jump Completion
4. Memory Read Access, Memory Write Completion or R-type Instruction Completion
5. Memory Read Completion (**Write Back**)

INSTRUCTIONS TAKE FROM 3 - 5 CYCLES!

Step 1: Instruction Fetch


- ❑ Use PC to get instruction from the memory and put it in the Instruction Register
- ❑ Increment the PC by 4 and put the result back in the PC
- ❑ Can be described succinctly using the RTL "Register-Transfer Language"

```
IR = Memory[PC];  
PC = PC + 4;
```

Can we figure out the values of the control signals?

What is the advantage of updating the PC now?

Datapath Activity During Instruction Fetch

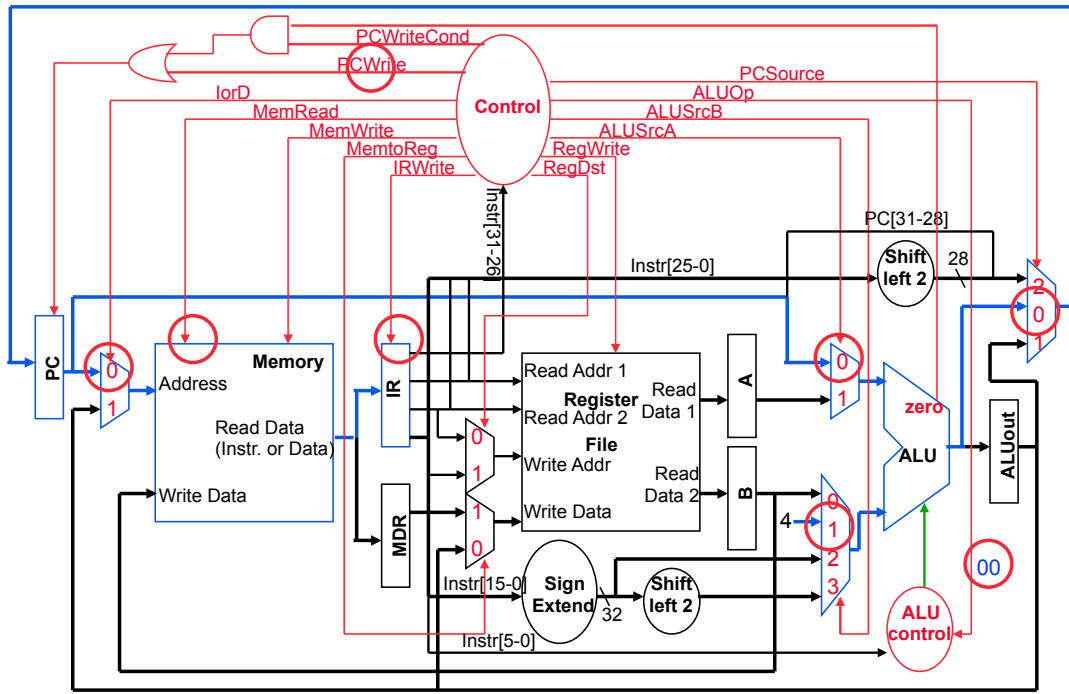

Page 15

Bressoud Spring 2010

Fetch Control Signals Settings

Unless otherwise assigned

start →

Instr Fetch

IorD=0
 MemRead; IRWrite
 ALUSrcA=0
 ALUSrcB=01
 PCSource, ALUOp=00
 PCWrite
 others=X

Page 17

Bressoud Spring 2010

Step 2: Instruction Decode and Register Fetch

- ❑ Don't know what the instruction is yet, so can only
 - Read registers rs and rt **in case** we need them
 - Compute the branch address **in case** the instruction is a branch
- ❑ The RTL:


```

A = Reg[IR[25-21]];
B = Reg[IR[20-16]];
ALUOut = PC
          +(sign-extend(IR[15-0]) << 2);


```

- ❑ Note we aren't setting any control lines based on the instruction (since we don't know what it is (the control logic is busy "**decoding**" the op code bits))

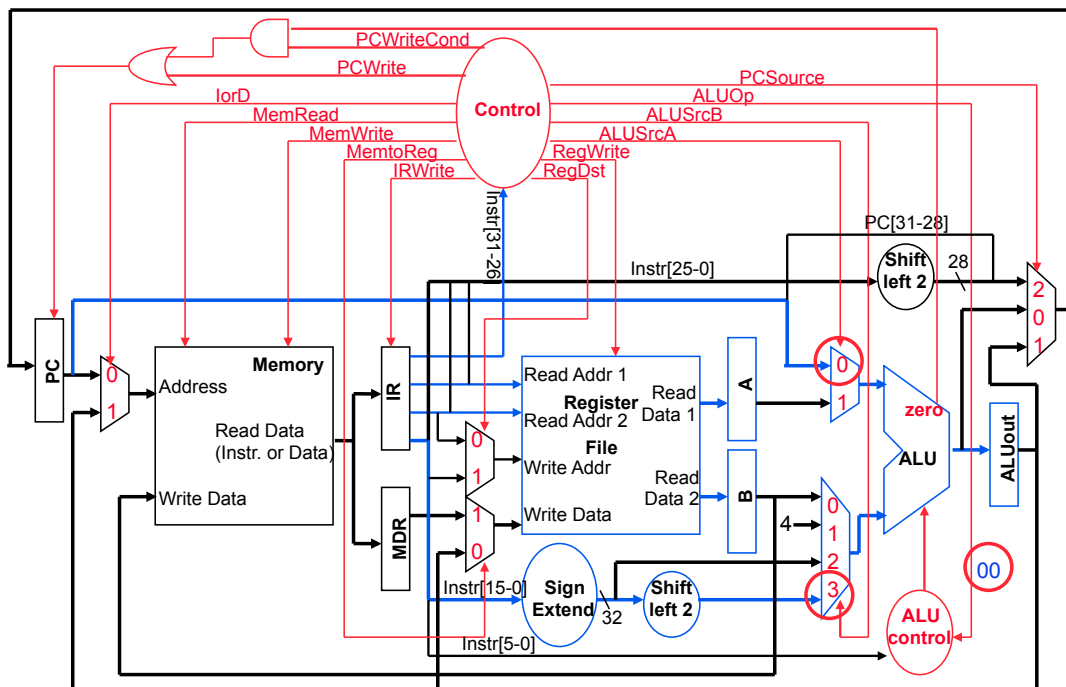Datapath Activity During Instruction Decode




Decode Control Signals Settings

 

Step 3 (instruction dependent)

- ❑ ALU is performing one of four functions, based on instruction type
- ❑ Memory reference (lw and sw):
$$\text{ALUOut} = A + \text{sign-extend}(\text{IR}[15-0]);$$
- ❑ R-type:
$$\text{ALUOut} = A \text{ op } B;$$
- ❑ Branch:
$$\text{if } (A == B) \text{ PC} = \text{ALUOut};$$
- ❑ Jump:
$$\text{PC} = \text{PC}[31-28] \parallel (\text{IR}[25-0] \ll 2);$$


Datapath Activity During lw & sw Execute

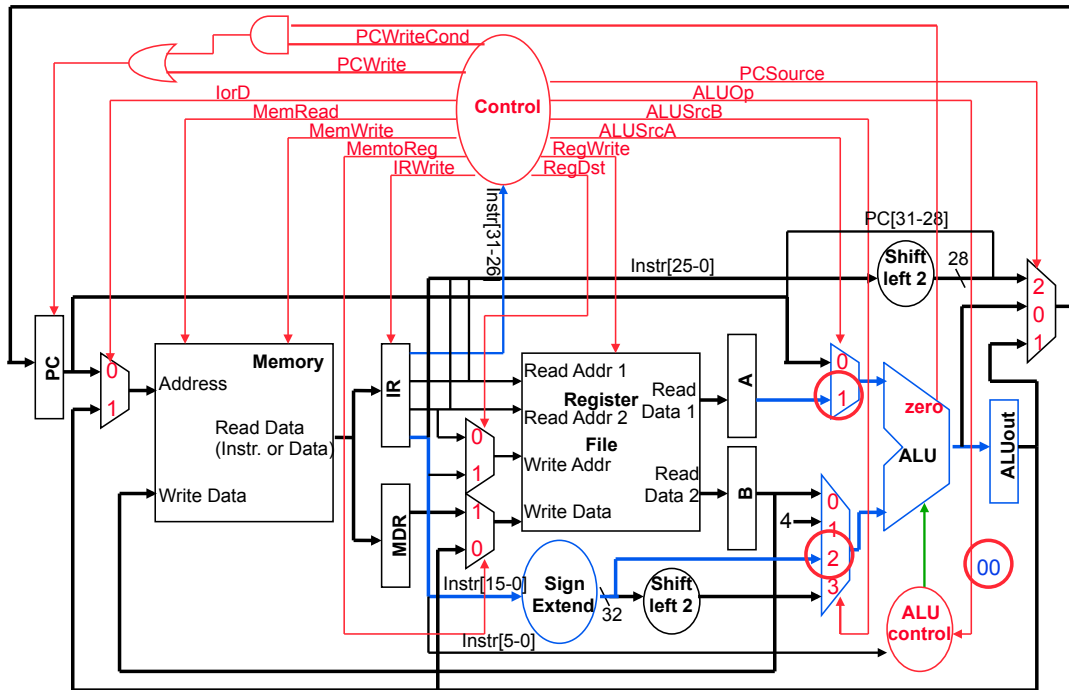

Page 25

Bressoud Spring 2010


Datapath Activity During R-type Execute

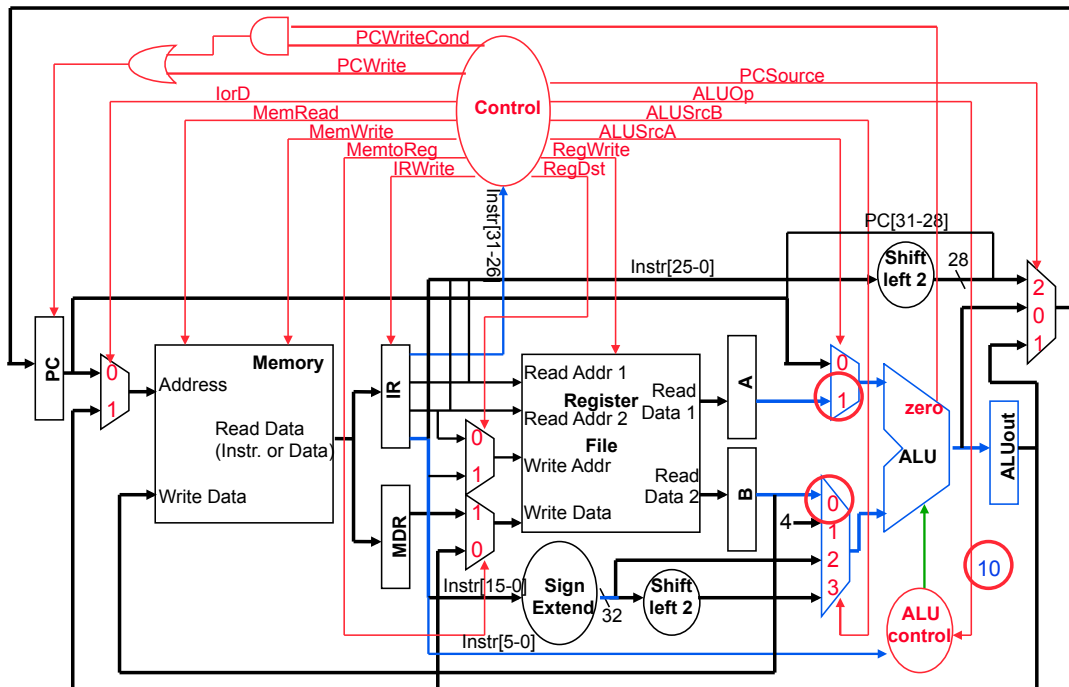

Page 27

Bressoud Spring 2010


Datapath Activity During beq Execute

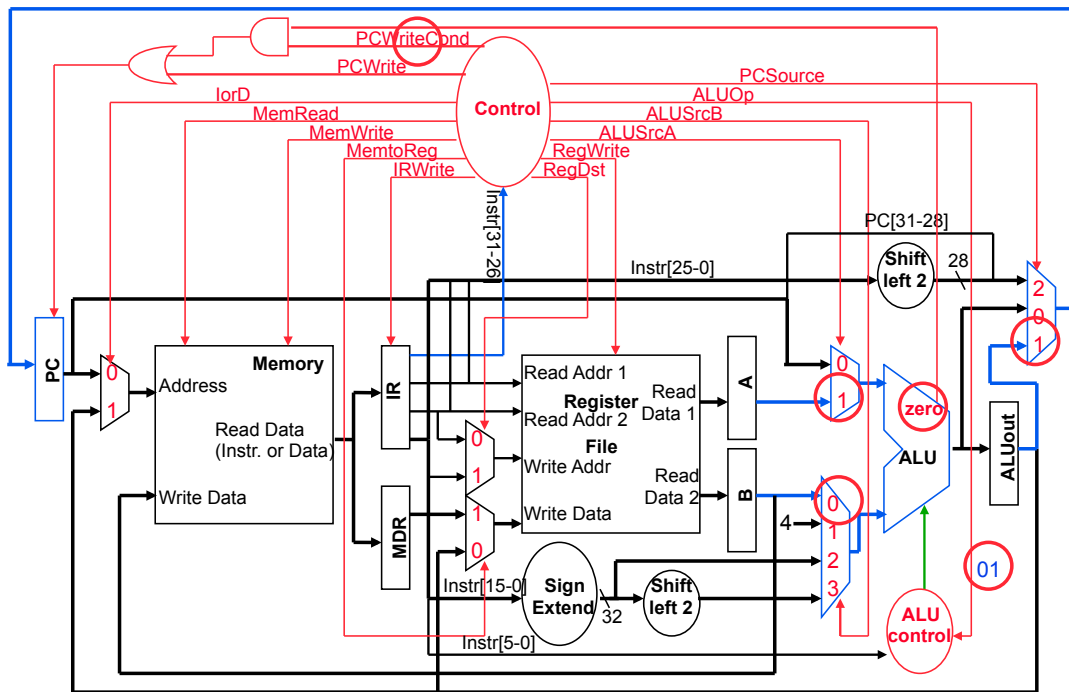

Page 29

Bressoud Spring 2010


Datapath Activity During j Execute

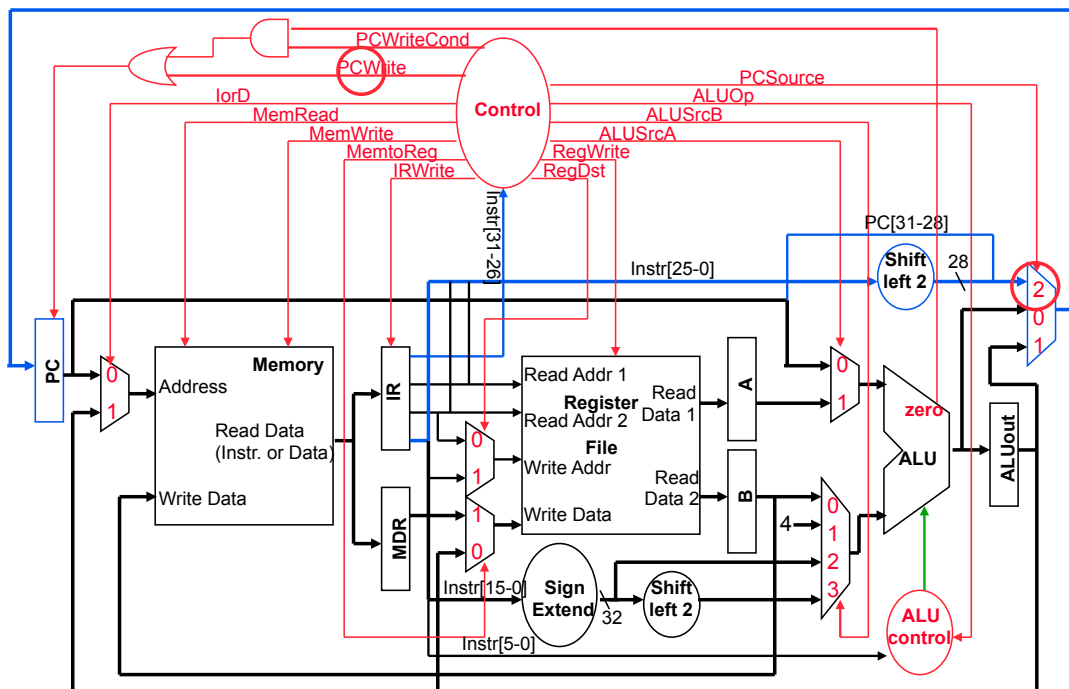

Page 31

Bressoud Spring 2010

Execute Control Signals Settings

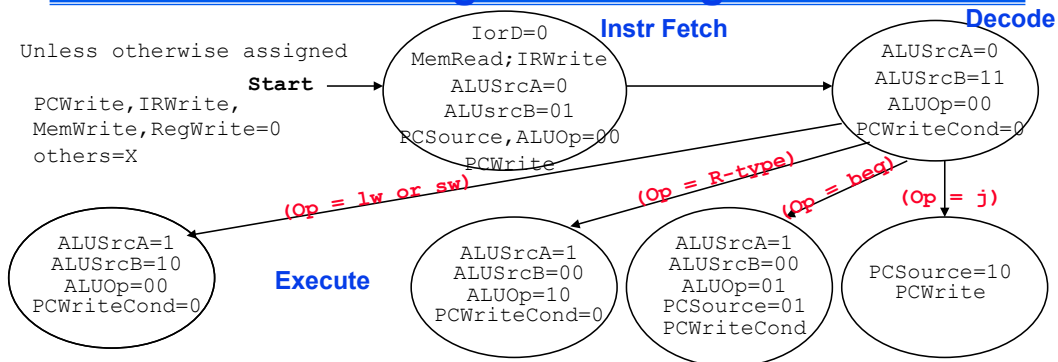

Step 4 (also instruction dependent)

❑ Memory reference:

MDR = Memory[ALUOut]; -- lw

or


Memory[ALUOut] = B; -- sw

❑ R-type instruction completion

Reg[IR[15-11]] = ALUOut;

❑ Remember, the register write actually takes place at the **end** of the cycle on the clock edge


Datapath Activity During **lw** Memory Access

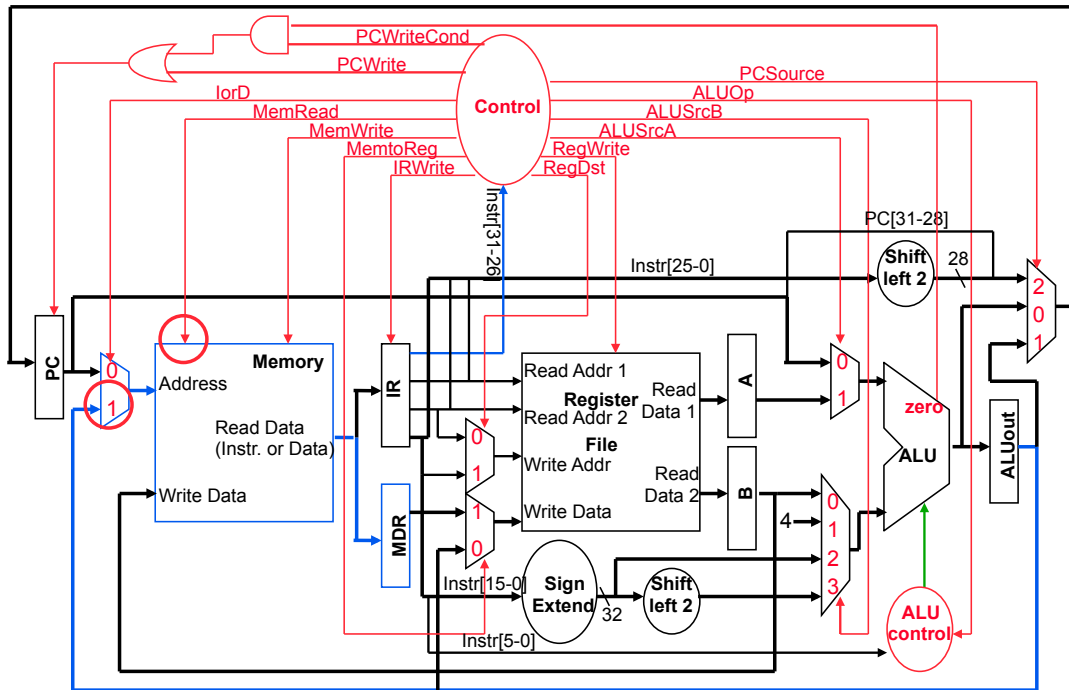

Page 36

Bressoud Spring 2010


Datapath Activity During **sw** Memory Access

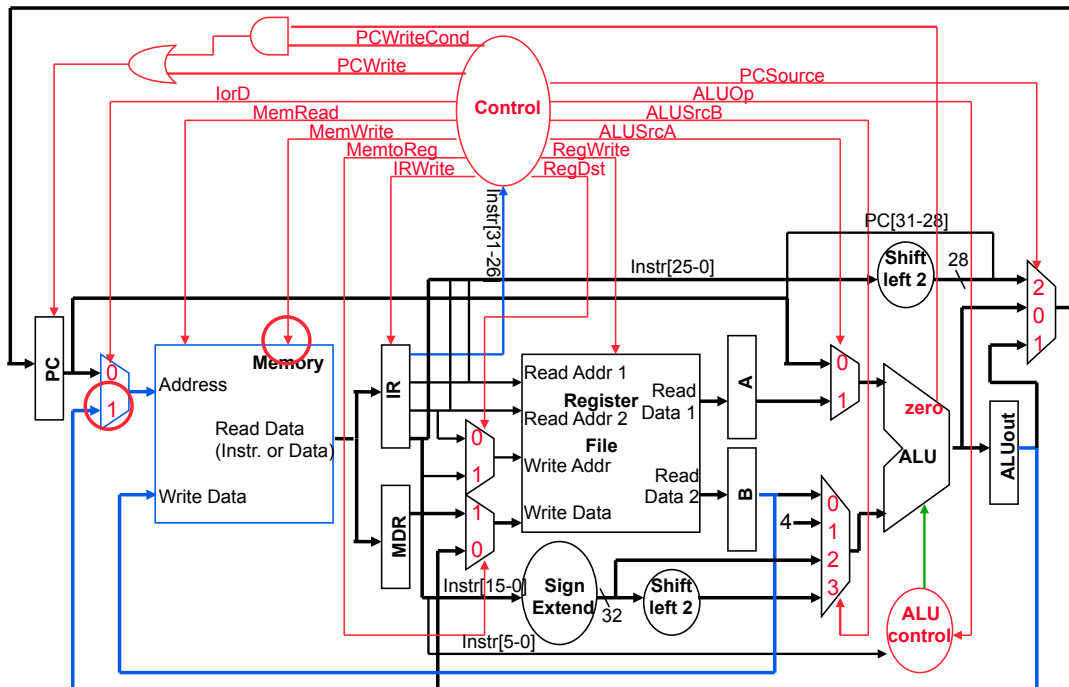

Page 38

Bressoud Spring 2010


Datapath Activity During R-type Completion

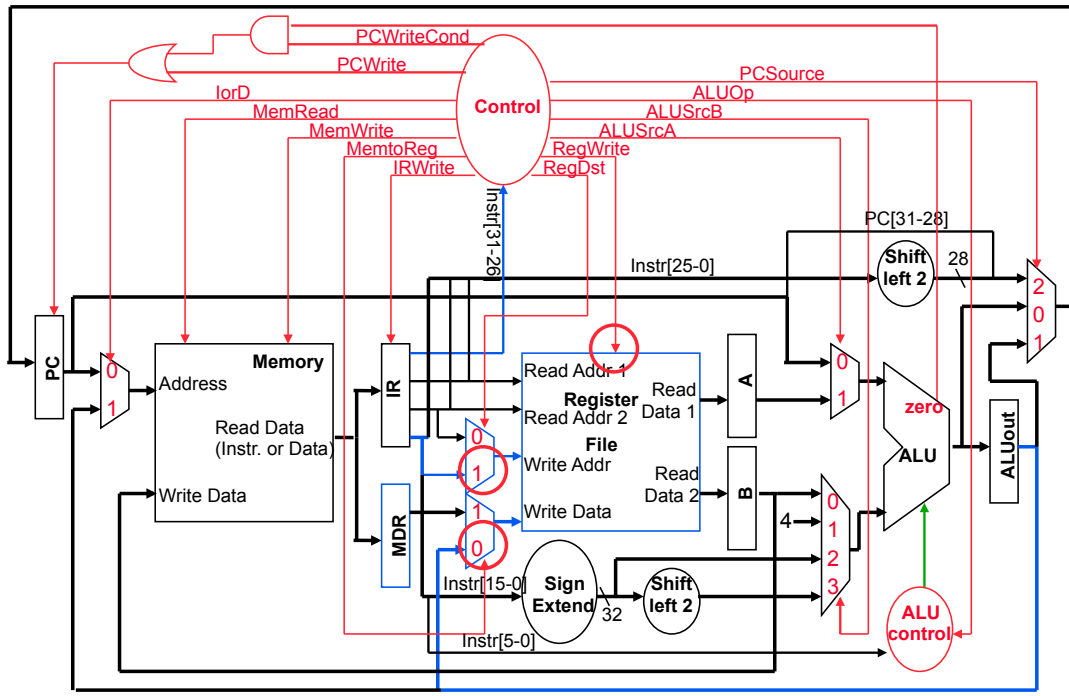

Page 40

Bressoud Spring 2010

Memory Access Control Signals Settings

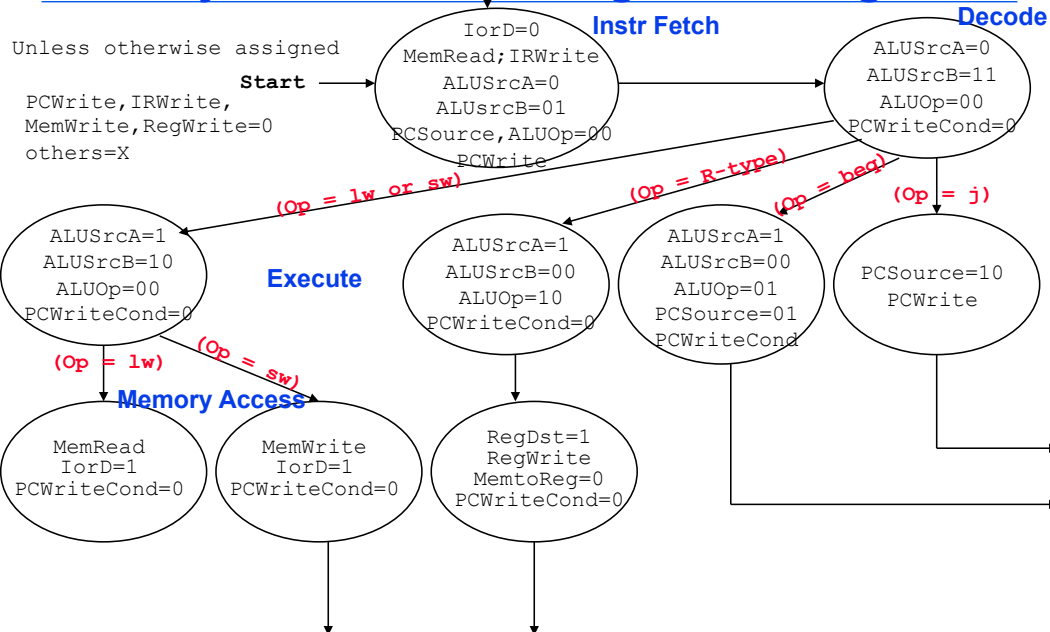

Page 42

Bressoud Spring 2010


Step 5: Memory Read Completion (Write Back)

- ❑ All we have left is the write back into the register file the data just read from memory for lw instruction


```
Reg[IR[20-16]] = MDR;
```

What about all the other instructions?

Datapath Activity During 1w Write Back

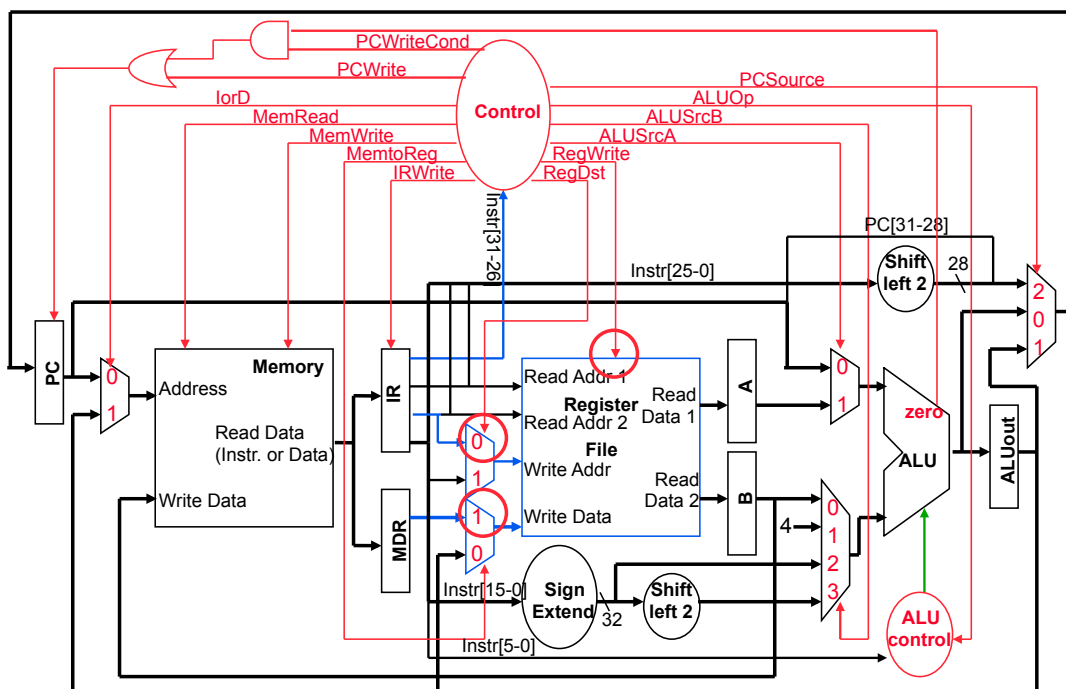

Write Back Control Signals Settings

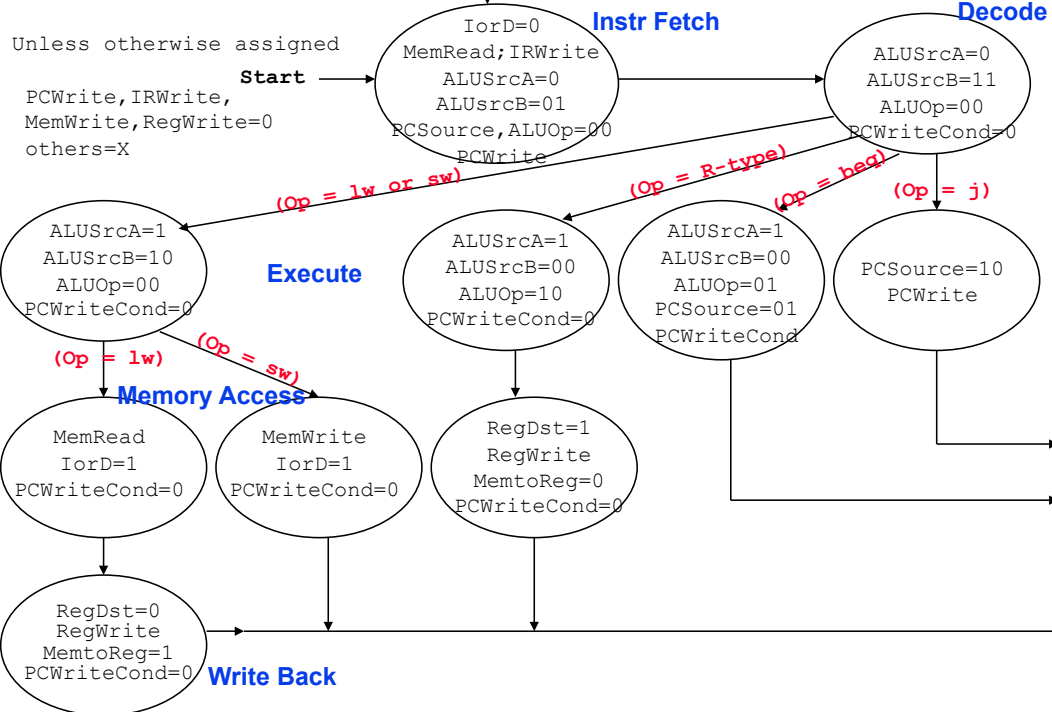

Page 47

Bressoud Spring 2010

RTL Summary

| Step | R-type | Mem Ref | Branch | Jump |
|---------------|---|--|------------------------|--------------------------------------|
| Instr fetch | IR = Memory[PC]; PC = PC + 4; | | | |
| Decode | A = Reg[IR[25-21]]; B = Reg[IR[20-16]]; ALUOut = PC + (sign-extend(IR[15-0]) << 2); | | | |
| Execute | ALUOut = A op B; | ALUOut = A + sign-extend(IR[15-0]); | if (A==B) PC = ALUOut; | PC = PC [31-28] (IR [25-0] << 2); |
| Memory access | Reg[IR [15-11]] = ALUOut; | MDR = Memory[ALUOut]; or Memory[ALUOut] = B; | | |
| Write-back | | Reg[IR[20-16]] = MDR; | | |

Page 48

Bressoud Spring 2010

Answering Simple Questions


- ❑ How many cycles will it take to execute this code?

```
lw    $t2, 0($t3)    5
lw    $t3, 4($t3)    5
beq   $t2, $t3, Label 3
#assume not
add   $t5, $t2, $t3   4
sw    $t5, 8($t3)     4
Label: ...           =
                                21 cycles
address for second lw being calculated
```


- ❑ What is going on during the 8th cycle of execution?
- ❑ In what cycle does the actual addition of \$t2 and \$t3 takes place? 16th cycle 12th cycle
- ❑ In what cycle is the branch target address calculated?

Multicycle Control


- ❑ Multicycle datapath control signals are not determined solely by the bits in the instruction
 - e.g., op code bits tell what operation the ALU should be doing, but *not* what instruction cycle is to be done next
- ❑ We can use a finite state machine for control
 - a set of states (current state stored in State Register)
 - next state function (determined by current state and the input)
 - output function (determined by current state)
- ❑ So we are using a **Moore** machine (datapath control signals based only on current state)

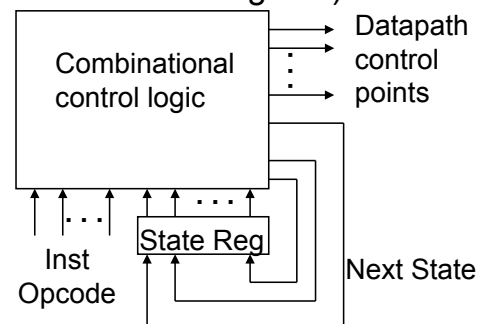

Multicycle Datapath Finite State Machine

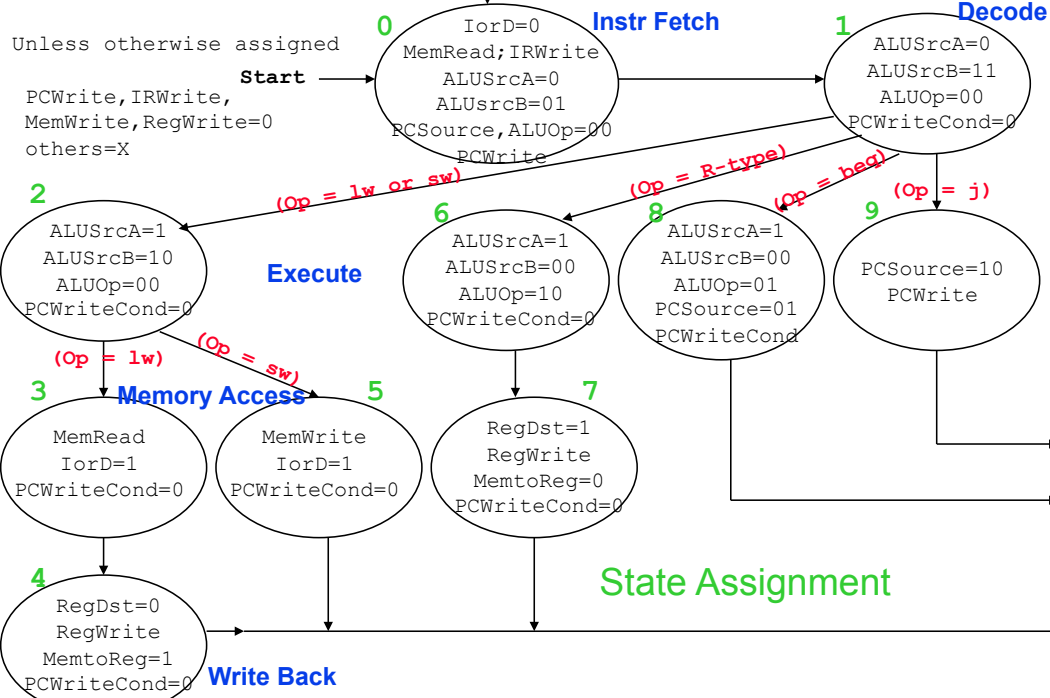

Finite State Machine Implementation

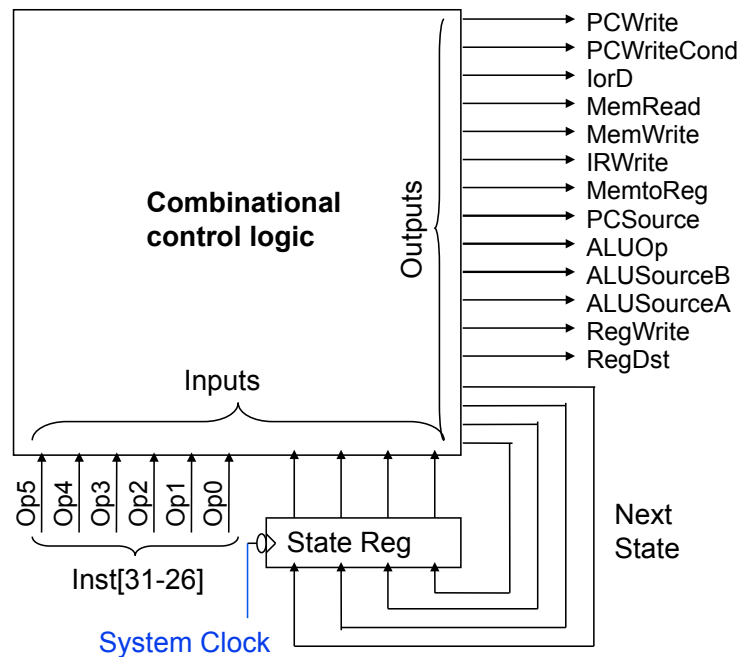

Datapath Control Outputs Truth Table

| Outputs | Input Values (Current State[3-0]) | | | | | | | | | |
|-------------|-----------------------------------|------|------|------|------|------|------|------|------|------|
| | 0000 | 0001 | 0010 | 0011 | 0100 | 0101 | 0110 | 0111 | 1000 | 1001 |
| PCWrite | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| PCWriteCond | X | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | X |
| IorD | 0 | X | X | 1 | X | 1 | X | X | X | X |
| MemRead | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| MemWrite | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| IRWrite | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| MemtoReg | X | X | X | X | 1 | X | X | 0 | X | X |
| PCSource | 00 | XX | XX | XX | XX | XX | XX | XX | 01 | 10 |
| ALUOp | 00 | 00 | 00 | XX | XX | XX | 10 | XX | 01 | XX |
| ALUSrcB | 01 | 11 | 10 | XX | XX | XX | 00 | XX | 00 | XX |
| ALUSrcA | 0 | 0 | 1 | X | X | X | 1 | X | 1 | X |
| RegWrite | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| RegDst | X | X | X | X | 0 | X | X | 1 | X | X |

Page 54

Bressoud Spring 2010

Next State Truth Table

| Current State [3-0] | Inst[31-26] (Op[5-0]) | | | | | |
|---------------------|-----------------------|--------------|--------------|-------------|-------------|-----------|
| | 000000 (R-type) | 000010 (jmp) | 000100 (beq) | 100011 (lw) | 101011 (sw) | Any other |
| 0000 | 0001 | 0001 | 0001 | 0001 | 0001 | 0001 |
| 0001 | 0110 | 1001 | 1000 | 0010 | 0010 | illegal |
| 0010 | XXXX | XXXX | XXXX | 0011 | 0101 | illegal |
| 0011 | XXXX | XXXX | XXXX | 0100 | XXXX | illegal |
| 0100 | XXXX | XXXX | XXXX | 0000 | XXXX | illegal |
| 0101 | XXXX | XXXX | XXXX | XXXX | 0000 | illegal |
| 0110 | 0111 | XXXX | XXXX | XXXX | XXXX | illegal |
| 0111 | 0000 | XXXX | XXXX | XXXX | XXXX | illegal |
| 1000 | XXXX | XXXX | 0000 | XXXX | XXXX | illegal |
| 1001 | XXXX | 0000 | XXXX | XXXX | XXXX | illegal |

Page 55

Bressoud Spring 2010

Simplifying the Control Unit Design

- ❑ For an implementation of the full MIPS ISA instr's can take from 3 clock cycles to 20+ clock cycles
 - resulting in finite state machines with hundreds to thousands of states with even *more* arcs (state sequences)
 - Such state machine representations become impossibly complex
- ❑ Instead, can represent the set of control signals that are asserted during a state as a low-level control “instruction” to be executed by the datapath

microinstructions
- ❑ “Executing” the microinstruction is equivalent to asserting the control signals specified by the microinstruction

Microprogramming

- ❑ A microinstruction has to specify
 - what control signals should be asserted
 - what microinstruction should be executed next
- ❑ Each microinstruction corresponds to one state in the FSM and is assigned a state number (or “address”)
 1. **Sequential** behavior – increment the state (address) of the current microinstruction to get to the state (address) of the next
 2. **Jump** to the microinstruction that begins execution of the next MIPS instruction (state 0)
 3. **Branch** to a microinstruction based on control unit input using dispatch tables
 - need one for microinstructions following state 1
 - need another for microinstructions following state 2
- ❑ The set of microinstructions that define a MIPS assembly language instruction (**macroinstruction**) is its **microroutine**

Defining a Microinstruction Format

- ❑ **Format** – the fields of the microinstruction and the control signals that are affected by each field
 - control signals specified by a field usually have functions that are related
 - format is chosen to simplify the representation and to make it difficult to write inconsistent microinstructions
 - i.e., that allow a given control signal be set to two different values
- ❑ Make each field of the microinstruction responsible for specifying a **nonoverlapping** set of control signals
 - signals that are never asserted simultaneously may share the same field
 - seven fields for our simple machine
 - ALU control; SRC1; SRC2; Register control; Memory; PCWrite control; Sequencing

Our Microinstruction Format

| Field | Value | Signal setting | Comments |
|------------------|-----------|------------------------------------|---|
| ALU control | Add | ALUOp = 00 | Cause ALU to add |
| | Subt | ALUOp = 01 | Cause ALU to subtract (compare op for beq) |
| | Func code | ALUOp = 10 | Use IR function code to determine ALU control |
| SRC1 | PC | ALUSrcA = 0 | Use PC as top ALU input |
| | A | ALUSrcA = 1 | Use reg A as top ALU input |
| SRC2 | B | ALUSrcB = 00 | Use reg B as bottom ALU input |
| | 4 | ALUSrcB = 01 | Use 4 as bottom ALU input |
| | Extend | ALUSrcB = 10 | Use sign ext output as bottom ALU input |
| | Extshft | ALUSrcB = 11 | Use shift-by-two output as bottom ALU input |
| Register control | Read | | Read RegFile using rs and rt fields of IR as read addr's; put data into A and B |
| | Write ALU | RegWrite, RegDst = 1, MemtoReg = 0 | Write RegFile using rd field of IR as write addr and ALUOut as write data |
| | Write MDR | RegWrite, RegDst = 0, MemtoReg = 1 | Write RegFile using rt field of IR as write addr and MDR as write data |

Our Microinstruction Format, con't

| Field | Value | Signal setting | Comments |
|------------------|--------------|-------------------------------|---|
| Memory | Read PC | MemRead, lorD = 0,IRWrite | Read memory using PC as addr; write result into IR (and MDR) |
| | Read ALU | MemRead, lorD = 1 | Read memory using ALUOut as addr; write results into MDR |
| | Write ALU | MemWrite, lorD = 1 | Write memory using ALUOut as addr and B as write data |
| PC write control | ALU | PCSource = 00 PCWrite | Write PC with output of ALU |
| | ALUOut-cond | PCSource = 01, PCWriteCond | If Zero output of ALU is true, write PC with the contents of ALUOut |
| | Jump address | PCSource = 10, PCWrite | Write PC with IR jump address after shift-by-two |
| Sequencing | Seq | AddrCtl = 11 | Choose next microinstruction sequentially |
| | Fetch | AddrCtl = 00 | Jump to the first microinstruction (i.e., Fetch) to begin a new instruction |
| | Dispatch 1 | AddrCtl = 01 | Branch using PLA_1 |
| | Dispatch 2 | AddrCtl = 10 | Branch using PLA_2 |

Page 60

Bressoud Spring 2010

Creating the Microprogram

❑ Fetch microinstruction

| Label (Addr) | ALU control | SRC1 | SRC2 | Reg control | Memory | PCWrite control | Seq'ing |
|--------------|-------------|------|------|-------------|---------|-----------------|---------|
| Fetch (0) | Add | PC | 4 | | Read PC | ALU | Seq |

compute PC + 4

fetch instr into IR write ALU output into PC go to instr 1

❑ Label field represents the state (address) of the microinstruction

❑ Fetch microinstruction assigned state (address) 0

Page 62

Bressoud Spring 2010


The Entire Control Microprogram

| Addr | ALU control | SRC1 | SRC2 | Reg control | Memory | PCWrite control | Seq'ing |
|------|-------------|------|----------|-------------|-----------|-----------------|---------|
| 0 | Add | PC | 4 | | Read PC | ALU | Seq |
| 1 | Add | PC | Ext shft | Read | | | Disp 1 |
| 2 | Add | A | Extend | | | | Disp 2 |
| 3 | | | | | Read ALU | | Seq |
| 4 | | | | Write MDR | | | Fetch |
| 5 | | | | | Write ALU | | Fetch |
| 6 | Func code | A | B | | | | Seq |
| 7 | | | | Write ALU | | | Fetch |
| 8 | Subt | A | B | | | ALUOut-cond | Fetch |
| 9 | | | | | | Jump address | Fetch |

Page 63

Bressoud Spring 2010


Microcode Implementation

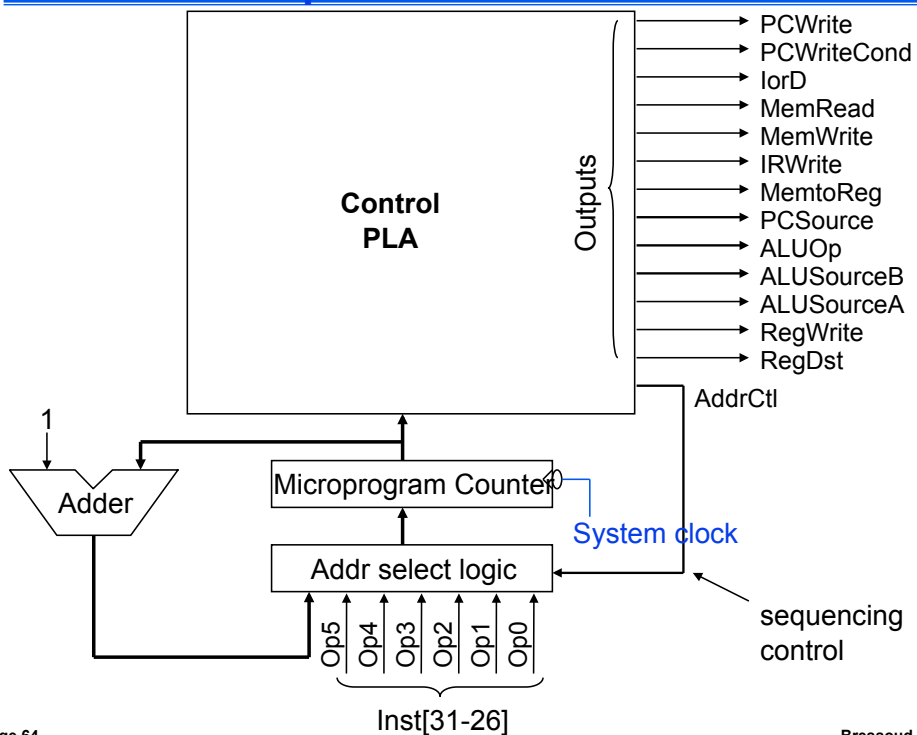

Page 64

Bressoud Spring 2010

Control Path Design Alternatives

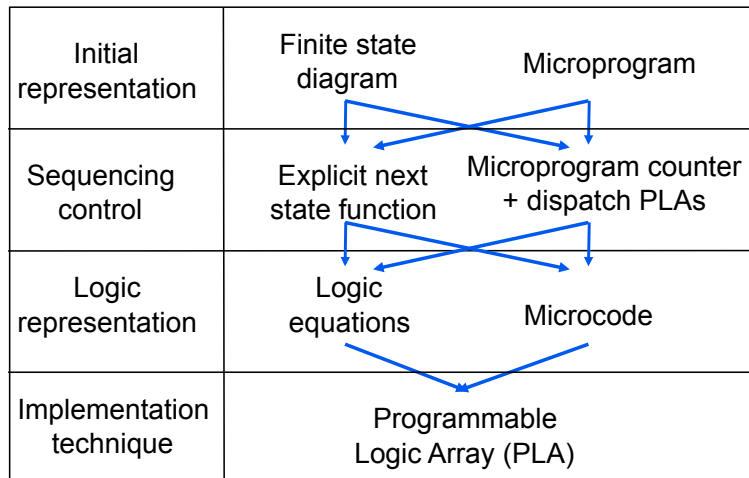


- ❑ Microprogram representation advantages
 - Easier to design, write, and debug

Multicycle Advantages & Disadvantages

- ❑ Uses the clock cycle efficiently – the clock cycle is timed to accommodate the slowest instruction **step**
 - balance the amount of work to be done in each step
 - restrict each step to use only one major functional unit
 - ❑ Multicycle implementations allow
 - faster clock rates
 - different instructions to take a different number of clock cycles
 - functional units to be used more than once per instruction as long as they are used on different clock cycles
- but
- ❑ Requires additional internal state registers, muxes, and more complicated (FSM) control

Single Cycle vs. Multiple Cycle Timing

Single Cycle Implementation:

 

Multiple Cycle Implementation:

